



# Computer Organization

---

## Lab11 CPU Design(3)


‘single’ cycle CPU  
clock, I/O



- A 'single' cycle CPU
- Clock (IP core)



- **MemOrIO**
- **Controller +**

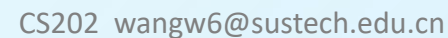



### 5-1) Decoder: write back the data




# Clock

➤ Add **PLL clock IP core** to generate the needed clock:

1. The clock on the Minisys/EGO1 development board is **100Mhz** *(clk\_in1)*  
➤ 100Mhz is too fast for a 'single' clock CPU

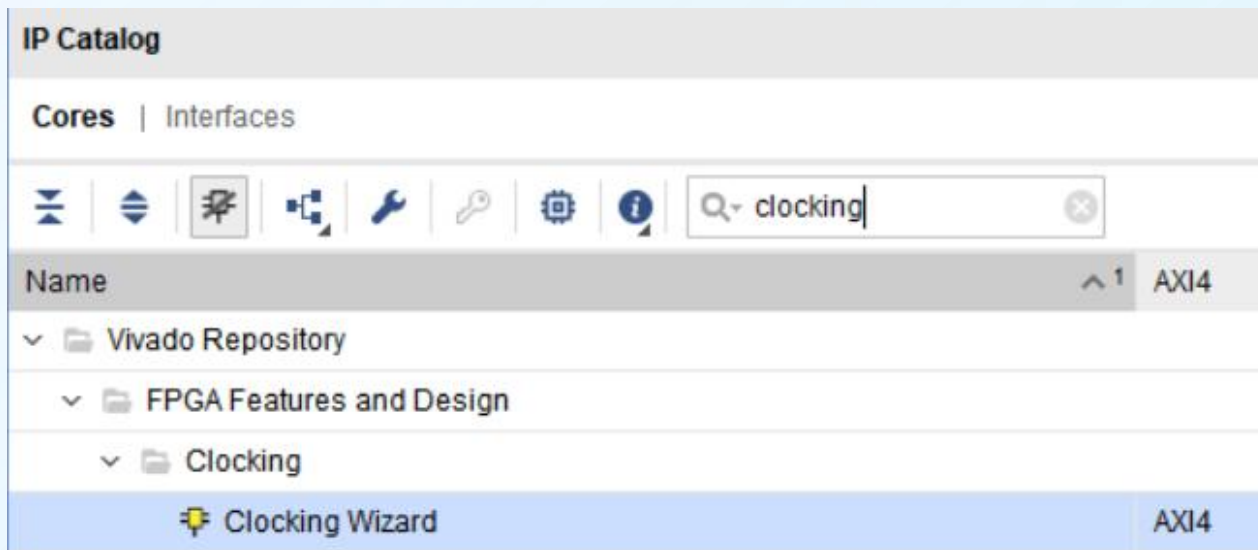2. A clock of 23Mhz is more suitable for the 'single' clock CPU *(clk\_out1)*







# Clock continued

Custom the IP core, set its **name**, **Primitive**, **Output Freq** and **with out the reset and locked**. Then **generate** the IP core with the settings.

Component Name **cpuck**

**Clocking Options** | Output Clocks | Port Renaming | PLL2 Settings | Summary

**Clock Monitor**

☐ Enable Clock Monitoring

**Primitive**

☐ MMCM ☒ **PLL**

**Clocking Features**

☒ Frequency Synthesis ☐ Minimize Power

☒ Phase Alignment

☐ Dynamic Reconfig

☐ Safe Clock Startup

**Jitter Optimization**

☒ Balanced

☐ Minimize Output Jitter

☐ Maximize Input Jitter filtering

**Clocking Options** | **Output Clocks** | Port Renaming | PLL2 Settings

The phase is calculated relative to the active input clock.

Output Clock	Port Name	Output Freq (MHz)	
		Requested	Actual
<input checked="" type="checkbox"/> clk_out1	clk_out1	23.000	23.000

Component Name **cpuck**

**Clocking Options** | **Output Clocks** | Port Renaming | PLL2 Settings | Summary

**Enable Optional Inputs / Outputs for MMCM/PLL**

☐ **reset** ☐ power\_down

☐ **locked**

**Reset Type**

☒ Active High ☐ Active Low



# The Function Verification of “cpuck”

Functional Verification by **testbench** and **simulator**

1) Create a verilog **testbench** module to instance the IP core “**cpuck**” and bind its ports. set the frequency of the input on “cpuck” as **100Mhz**.


2) Do the simulation to verify whether the output signal is a **23Mhz** clock signal while the input signal is **100Mhz**.

```
module cpuck_tb( ); // a reference testbench for 'cpuck'


    reg clk_in;
    wire clk_out;
    cpuck clk1( .clk_in1(clk_in), .clk_out1(clk_out) );

    initial      clk_in = 1'b0;
    always #5 clk_in=~clk_in;
endmodule
```

 **NOTE:** The output of IP core 'cpuck' need to work for a 'long' time to achieve stability.



# Build and test the CPU

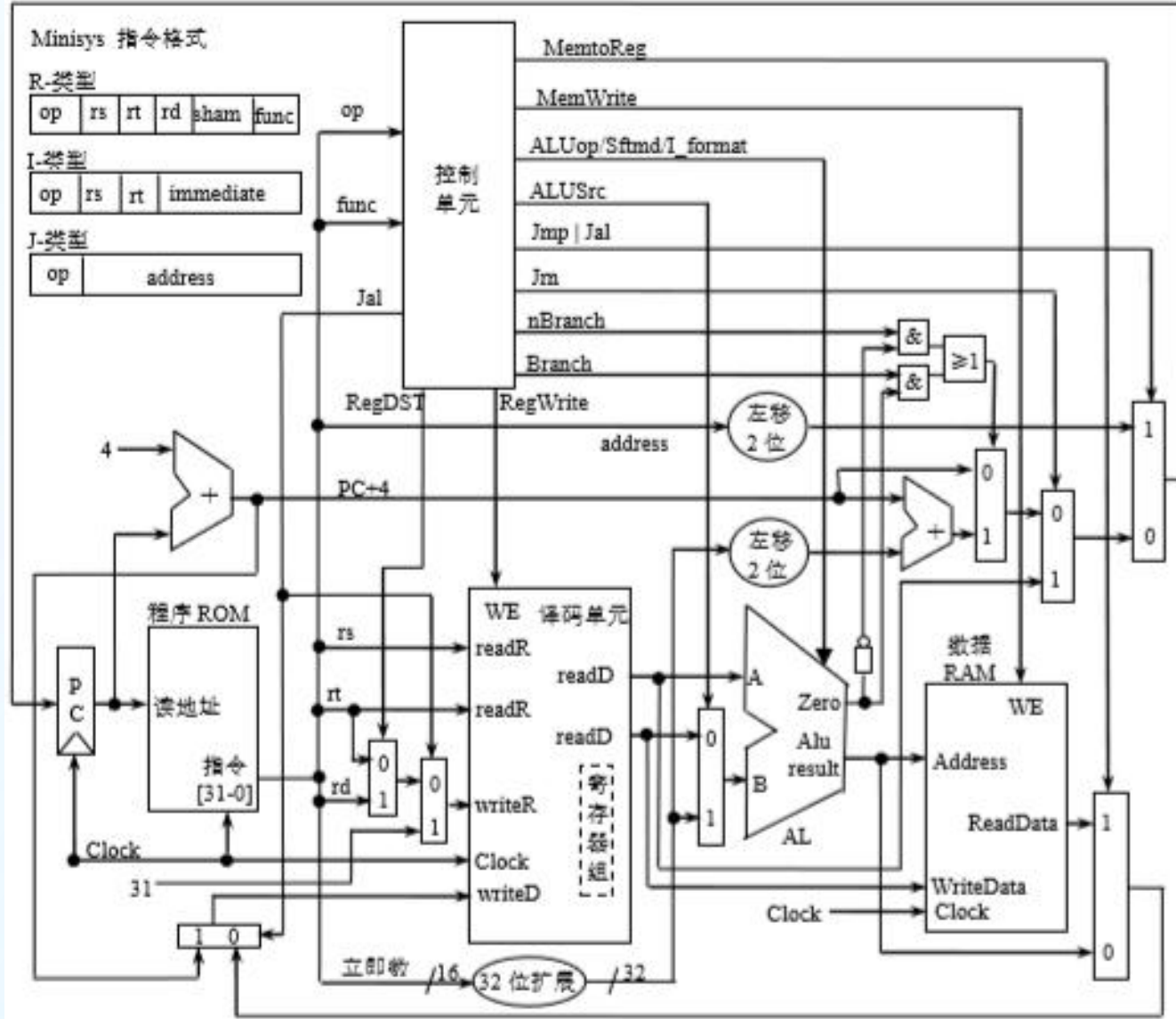

## Build a CPU top module

1) **Instantiating** the sub-modules: **clock**, **Decoder**, execution unit/**ALU**, **IFetch**, **Controller** and **Data-Memory**.

2) Complete the inter-module connection inside the CPU and the **binding** to the CPU port.


**Q1. How to test the CPU ?**  
**how to determine the**  
**program, the data, how to**  
**check the result?**






# I/O interface

Minisys board with FPGA chip embedded

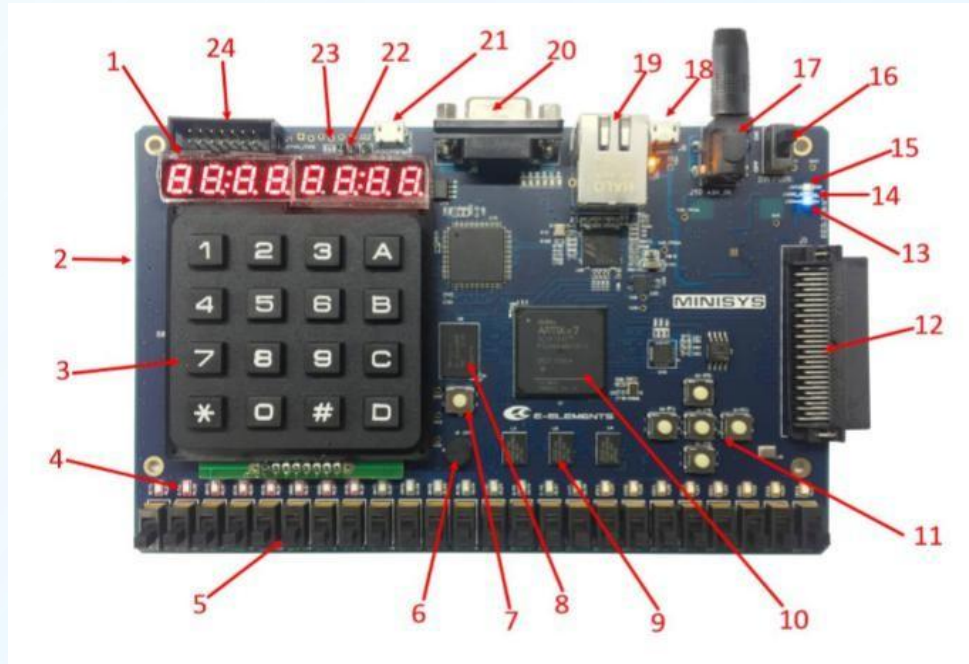

EGO1 board with FPGA chip embedded

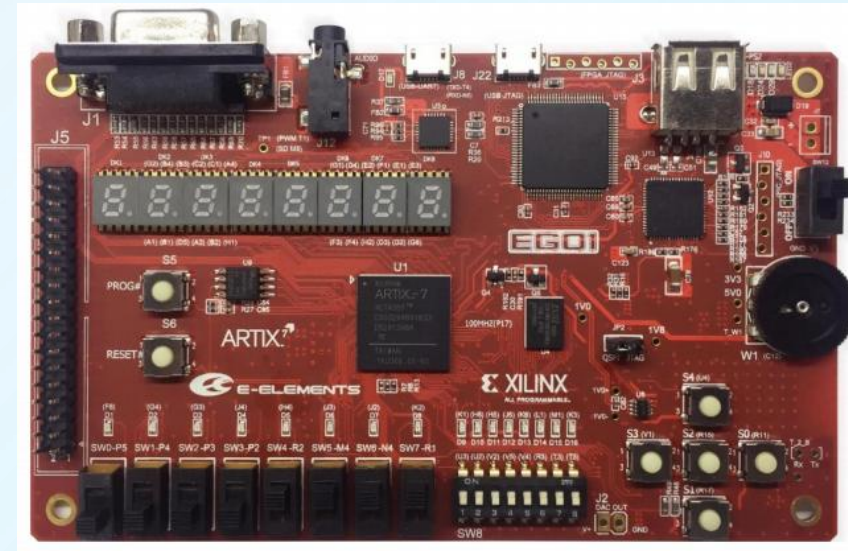

We have practiced a Cropped CPU on EGO1 in lab1



## TIPS:

The handbook of board **Minisys** and **EGO1** could be found in the directory "labs\Handbook\_of\_Minisys\_EGO1" on the course **BlackBoard** sit





# A Simple Design on the I/O Interface

This part mainly accomplishes the following work:


1. Add I/O function
2. 16-bit LED design
3. 16-bit DIP Switch design

This is only one of the design solutions for I/O related data bus. Please develop a solution that suits your design needs!
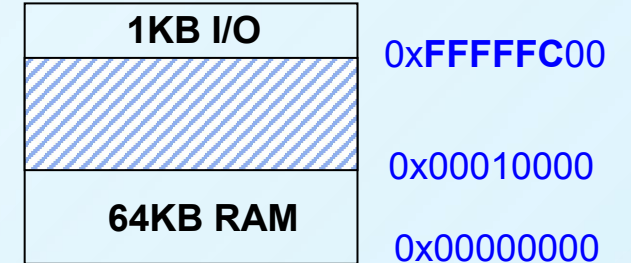
# I/O Share Part of the Data Bus Address

The space of **32** bits address bus is **4GB**(0x0000\_0000~0xFFFF\_FFFF)

**1024** bytes(0xFFFF\_FC00~0xFFFF\_FFFF) is designed to be allocated for the **I/O**.  
Chip **Select** and **address** are specified by specifying **10** IO port lines.



Here is an example for **24 LED lights** and **24 DIP switches** on Minisys board, both of them are divided into two groups, all the ports in one group share the same address.

1. The CS(Chip Select) signal of the LED light is **ledCtrl**
2. The CS(Chip Select) signal of the DIP switch is **switchCtrl**

Range	LED(1~16)	LED(17~24)	Switch(1~16)	Switch(17~24)
Address	0xFFFFFC60	0xFFFFFC62	0xFFFFFC70	0xFFFFFC72


## Note:

1. In the computer field, there are usually two schemes for I/O address space design: I/O and memory **unified addressing** or I/O **independent addressing**. However there is no dedicated I/O instruction in current Minisys-1. Here, both LW and SW instructions are used for RAM access and I/O access, which means Minisys-1 can only use I/O unified addressing.

2. It is just a way for IO address implementation (MMIO: Memory-Mapped Input Output) , but not the only choice.




# Corresponding Operation of LW/SW

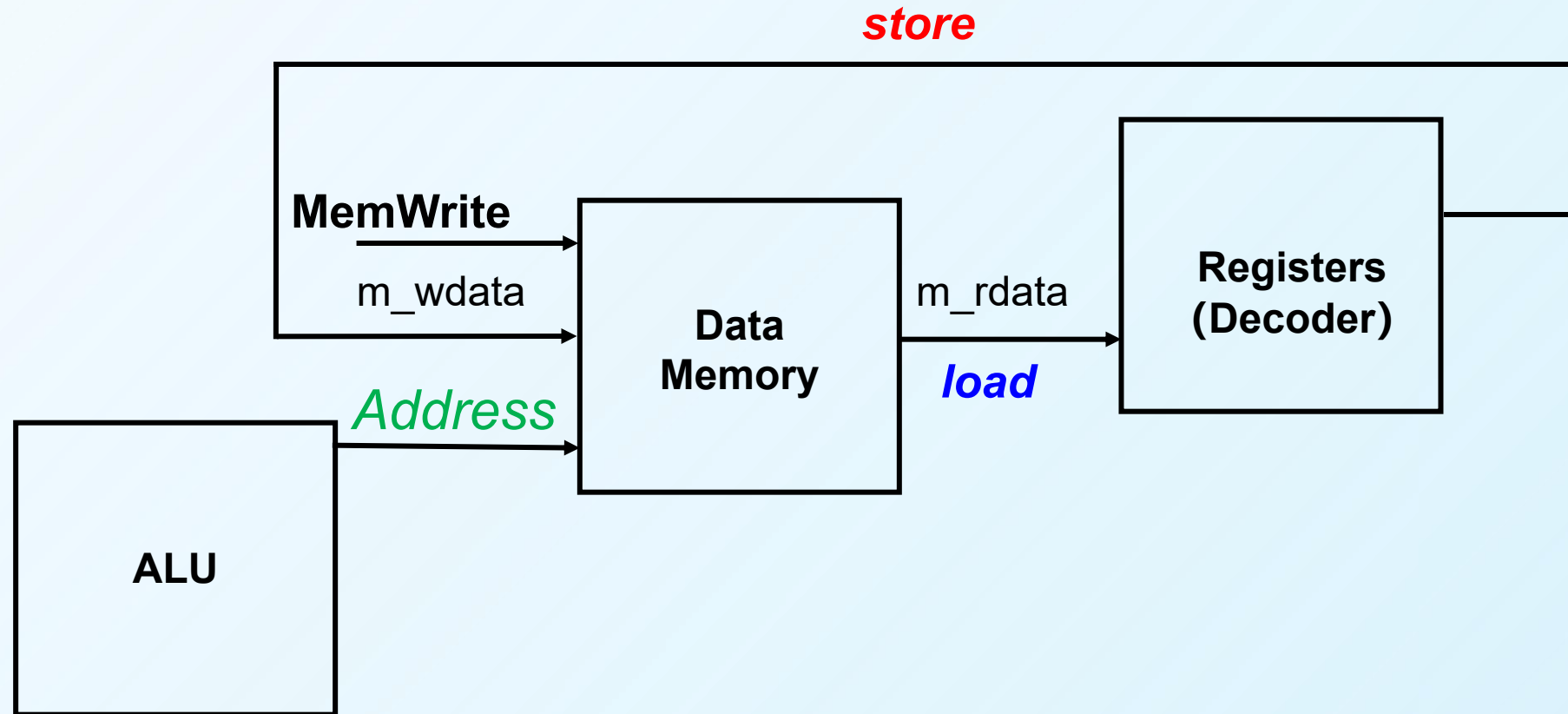


NOTE:

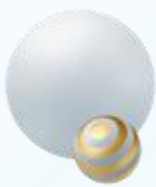- 1) There is no specific instruction in Minisys to read data from input ports and write data to output ports.
- 2) To implement the read/write process on I/O, it needs to **share the load/store instructions** in Minisys.




# MemOrIO

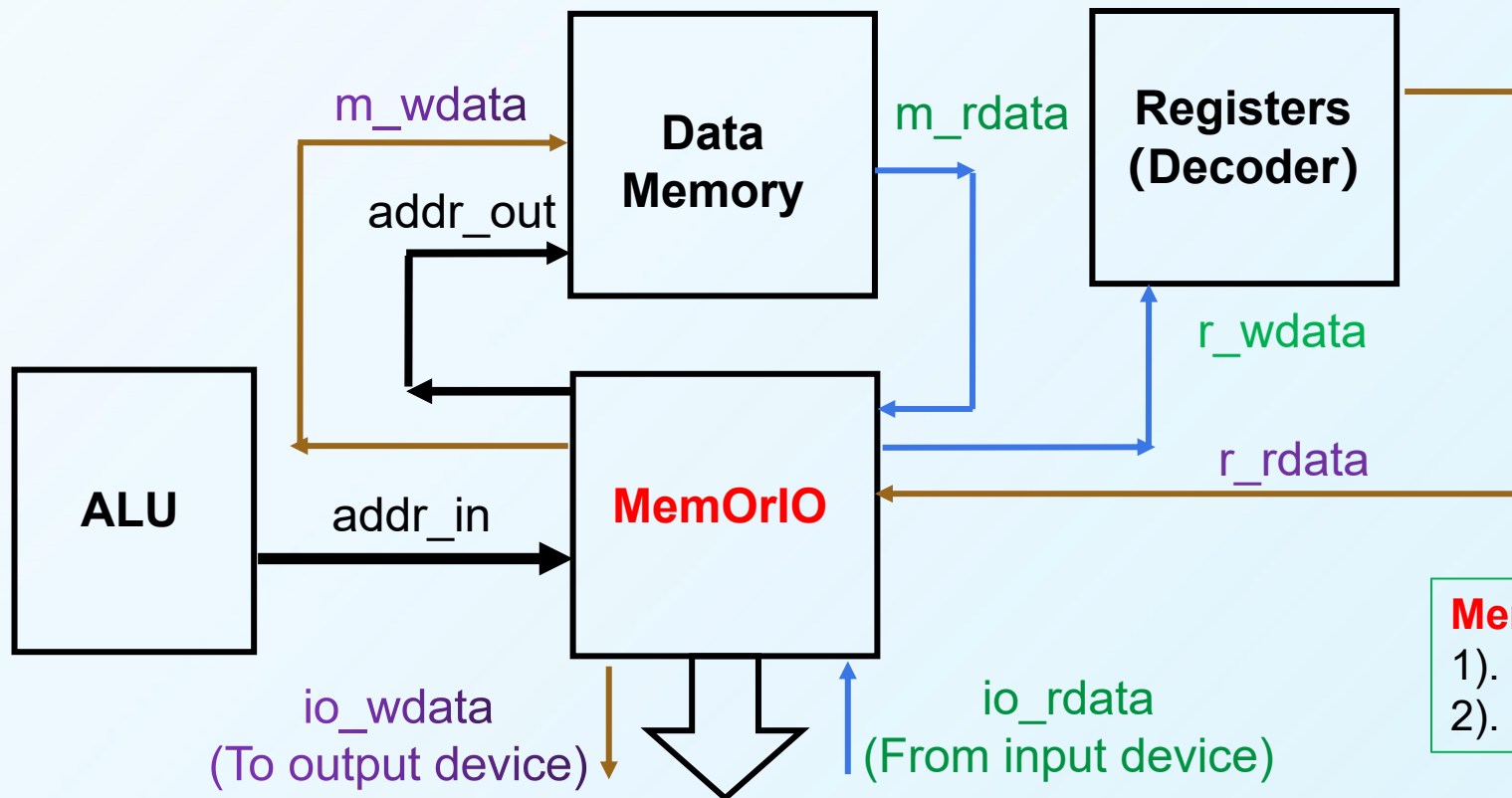

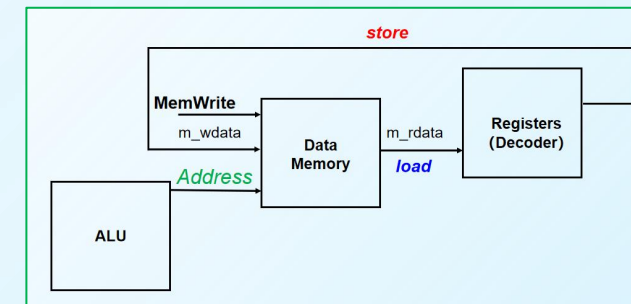**Chip Select signal**

**LedCtrl** (0xFFFFFC60, 0xFFFFFC62)

**SwitchCtrl** (0xFFFFFC70, 0xFFFFFC72)...




**MemOrIO** determine:

- 1). The source of **r\_wdata**
- 2). The destination of **r\_rdata**





# MemOrIO continued

 

```
module MemOrIO( mRead, mWrite, ioRead, ioWrite, addr_in, addr_out,
m_rdata, io_rdata, r_wdata, r_rdata, write_data, LEDCtrl, SwitchCtrl);

input mRead; // read memory, from Controller
input mWrite; // write memory, from Controller
input ioRead; // read IO, from Controller
input ioWrite; // write IO, from Controller

input[31:0] addr_in; // from alu_result in ALU
output[31:0] addr_out; // address to Data-Memory


input[31:0] m_rdata; // data read from Data-Memory
input[15:0] io_rdata; // data read from IO, 16 bits
output[31:0] r_wdata; // data to Decoder(register file)

input[31:0] r_rdata; // data read from Decoder(register file)
output reg[31:0] write_data; // data to memory or I/O (m_wdata, io_wdata)
output LEDCtrl; // LED Chip Select
output SwitchCtrl; // Switch Chip Select
```

*Tips: A demo about how the **Chip Select** signals work on I/O could be found in **labs/lab11\_io** on course BlackBoard site*



# MemOrIO continued

 

```
assign addr_out= addr_in;  
// The data write to register file may be from memory or io.  
// While the data is from io, it should be the lower 16bit of r_wdata.  
assign r_wdata = ? ? ?
```

```
// Chip select signal of Led and Switch are all active high;  
assign LEDCtrl= ? ? ?  
assign SwitchCtrl= ? ? ?
```


```
always @* begin  
    if((mWrite==1)||(ioWrite==1))  
        //write_data could go to either memory or IO. where is it from?  
        write_data = ? ? ?  
    else  
        write_data = 32'hZZZZZZZZ;  
end  
endmodule
```

# The Function Verification of MemOrIO

// a reference for the testbench of MemOrIO

```
module MemOrIO_tb( );
    reg mRead,mWrite,ioRead,ioWrite;
    reg[31:0] addr_in,m_rdata,r_rdata;
    reg[15:0] io_rdata;
    wire LEDCtrl,SwitchCtrl;
    wire [31:0] addr_out,r_wdata,write_data;
```
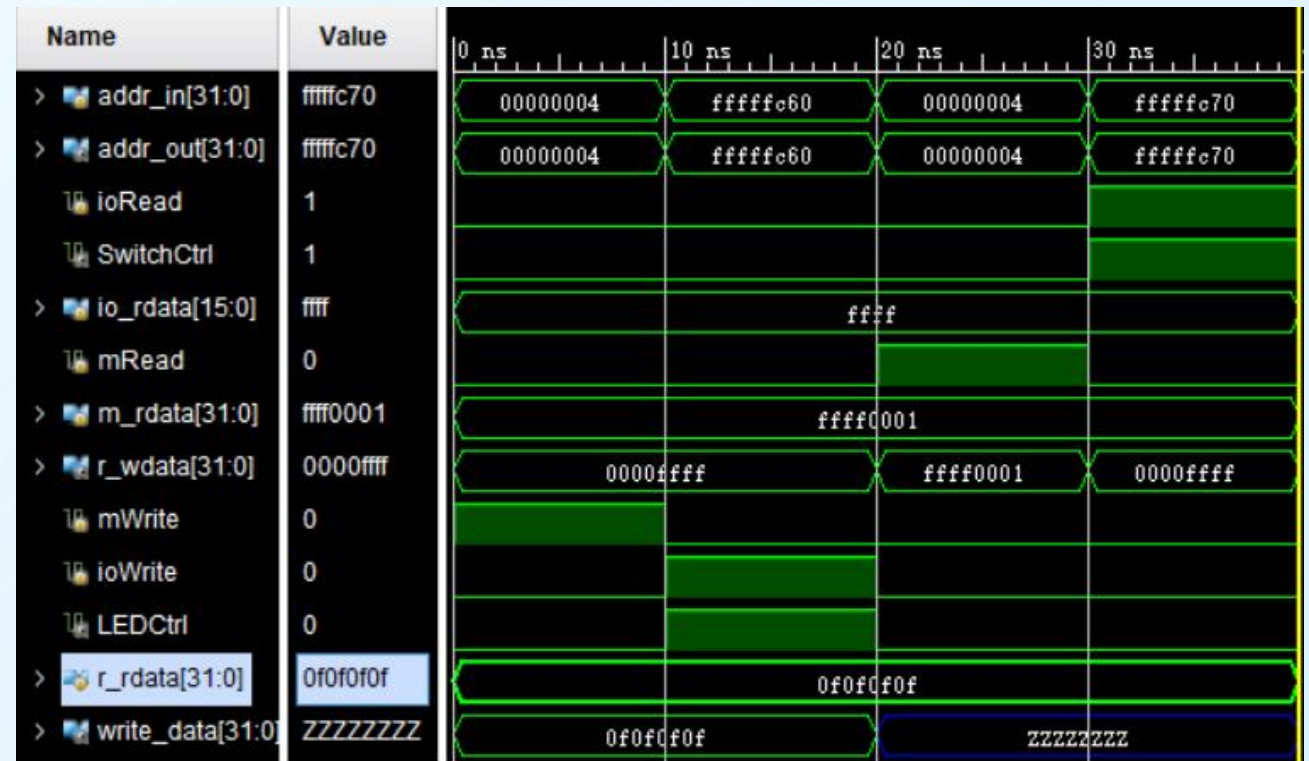
```
    MemoryOrIO umio(addr_out, addr_in,
        mRead, mWrite, ioRead, ioWrite,
        m_rdata, io_rdata, r_rdata, r_wdata, write_data,
        LEDCtrl, SwitchCtrl);
```




```
initial begin // r_rdata -> m_wdata(write_data)
    m_rdata = 32'h0xffff_0001; io_rdata = 16'h0xffff; r_rdata = 32'h0x0f0f_0f0f; addr_in = 32'h4;{mRead,mWrite,ioRead,ioWrite}= 4'b01_00;
    #10 addr_in = 32'hffff_fc60; {mRead,mWrite,ioRead,ioWrite}= 4'b00_01; // r_rdata -> io_wdata(write_data)
    #10 addr_in = 32'h0000_0004; {mRead,mWrite,ioRead,ioWrite}= 4'b10_00; // m_rdata -> r_wdata
    #10 addr_in = 32'hffff_fc70; {mRead,mWrite,ioRead,ioWrite}= 4'b00_10; // io_rdata -> r_wdata(write_data)
    #10 $finish;
end
endmodule
```


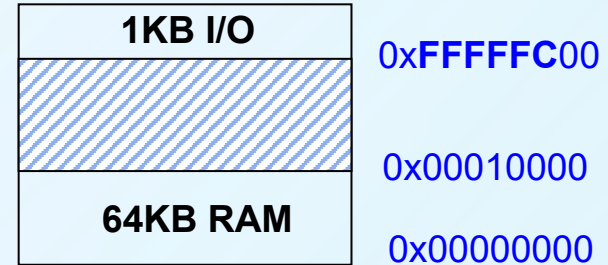
# Controller+

Add new ports to Controller for IO reading and writing support.



```
module control32(Opcode,Function_opcode,Jr,Branch,nBranch,Jmp,Jal,
Alu_resultHigh,
RegDST, MemorIOtoReg, RegWrite,
MemRead, MemWrite,
IORead, IOWrite,
ALUSrc,ALUOp,Sftmd,I_format);
...
input[21:0] Alu_resultHigh; // From the execution unit Alu_Result[31..10]
output MemorIOtoReg; // 1 indicates that data needs to be read from memory or I/O to the register
output RegWrite; // 1 indicates that the instruction needs to write to the register
output MemRead; // 1 indicates that the instruction needs to read from the memory
output MemWrite; // 1 indicates that the instruction needs to write to the memory
output IORead; // 1 indicates I/O read
output IOWrite; // 1 indicates I/O write
...
```





# Controller+ continued

- 1) **Modify** the logic of the '**MemWrite**'
- 2) **Add** '**MemRead**', '**IORead**' and '**IOWrite**' signals
- 3) **Change** '**MemtoReg**' to '**MemorIotoReg**'.

```
// The real address of LW and SW is Alu_Result, the signal comes from the execution unit
// From the execution unit Alu_Result[31..10], used to help determine whether to process Mem or IO
input[21:0] Alu_resultHigh;

output    MemorIotoReg;    //1 indicates that read data from memory or I/O to write to the register
output    MemRead;        // 1 indicates that reading from the memory to get data
output    IORead;         // 1 indicates I/O read
output    IOWrite;        // 1 indicates I/O write

assign RegWrite = (R_format || Lw || Jal || I_format) && !(Jr) ;    // Write memory or write IO
assign MemWrite = ((sw==1) && (Alu_resultHigh[21:0] != 22'h3FFFFFF)) ? 1'b1:1'b0;
assign MemRead = ? ? ?    // Read memory
assign IORead = ? ? ?    // Read input port
assign IOWrite = ? ? ?    // Write output port

// Read operations require reading data from memory or I/O to write to the register
assign MemorIotoReg = IORead || MemRead;
```



# Practice

P1-1. Do the functional verification on the module `cpuclk`(which is introduced in the first part of this lab)

P1-2. Answer the Q2 on page 2 and Q1 on page 7 of this lab slides.

P2. Complete the following modules, do the function verification:

- 1. MemoryOrIO
- 2. Controller+
- 3. Single cycle CPU with I/O process

P3. Redesign and implement the solution about I/O data bus and I/O addressing that are suitable for your design. Build the single cycle CPU with the updated solution of I/O process and do the function verification.